



70. If the ammeter in the circuit above reads zero, what is the resistance  $R$ ?
- (A)  $1.5\ \Omega$
  - (B)  $2\ \Omega$
  - (C)  $4\ \Omega$
  - (D)  $5\ \Omega$
  - (E)  $6\ \Omega$